

Amrita Vishwa Vidyapeetham  
Amrita School of Engineering , Amaravati  
B. Tech Mid-term Examinations Oct 2024  
1<sup>st</sup> Semester  
Computer and Communication Engineering  
23CCE102 Fundamentals of Electrical Engineering

Duration: Two hours

Maximum: 50 Marks

**Course Outcomes (COs):**

CO	Course Outcomes
CO01	understand fundamental electrical quantities
CO02	understand the principles of electrical measurements
CO03	analyse ac and dc circuits
CO04	understand the operation of electromagnetic machines


**Answer all the questions**

1. An apartment building has following average electrical consumptions per day:


- a. 4 CFL bulbs of 30W working for 5 hours
  - b. 3 filament lamps of 50W working 8 hours
  - c. One air conditioner of 1.5kW working 9 hours
  - d. one electric heater of 0.75kW working 1 hour
  - e. One television of 60W working for 6 hours
  - f. Washing machine of 0.7kW working for 1 hour
  - g. Pumping motor of 3kW working for 90 min
  - h. Refrigerator of 1kW working for 15 hours
- Estimate the cost of energy per month if one unit costs Rs. 6.25 that has to be paid for electricity board.

[10M] [CO01] [BTL3]

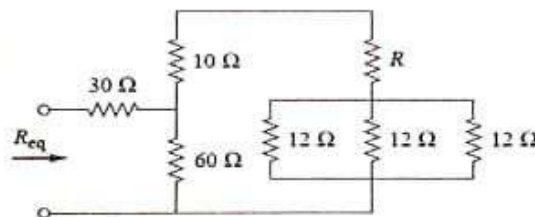2. a. If  $R_{eq} = 50 \text{ ohm}$  in the below circuit of find R.




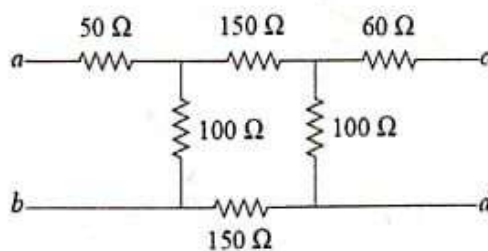b. Consider the circuit given below. Find the equivalent resistance at terminals: (a) a-b, (b) c-d.



[5+5=10M] [CO01] [BTL3]

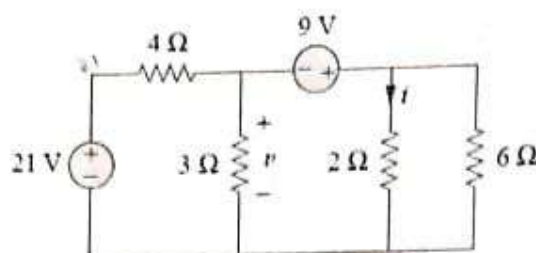
3. Find  $v$  and  $i$  in the circuit given below.



[10M] [CO02] [BTL3]


4. Use superposition theorem to obtain  $v_x$  in the below circuit.

[10M] [CO02] [BTL4]

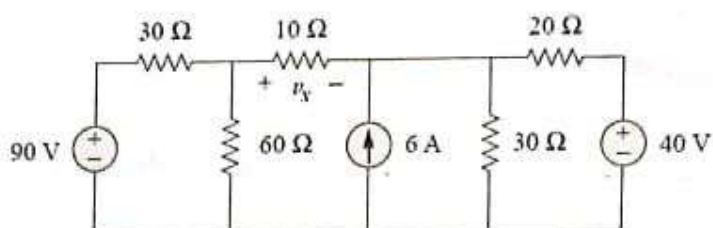

5. (a) For the circuit given below obtain the Thevenin equivalent at terminal a-b.  
 (b) Calculate the current in  $R_L=8\text{ Ohm}$   
 (c) Find  $R_L$  for maximum power deliverable to  $R_L$   
 (d) Determine that maximum power.

[10M] [CO03] [BTL2]

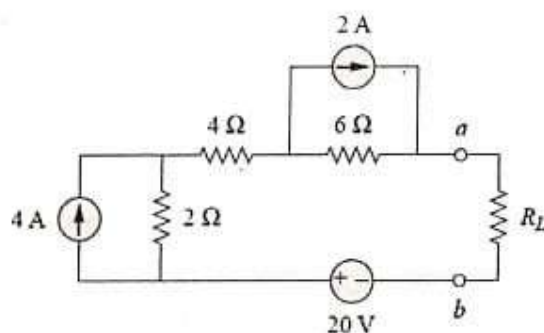

CO	Marks	BTL	Marks
CO01	20	BTL 1	0
CO02	20	BTL 2	10
CO03	10	BTL 3	30
		BTL 4	10

Course Outcome /Bloom's Taxonomy Level (BTL) Mark Distribution Table